

Short presentation

## **ESD protection devices**

Renesas Design Vietnam Co., Ltd.  
Circuit Design Group

Vuong Hoang

April 18<sup>th</sup>, 2014

# Outline

## 1. Overview of ESD

## 2. ESD protection devices

2.1 – Diode

2.2 – MOSFET

2.3 – Thick Field Oxide device - TFO

2.4 – Silicon Controlled Rectifier – SCR

## 3. Conclusion

# Outline

## 1. Overview of ESD

## 2. ESD protection devices


2.1 – Diode

2.2 – MOSFET

2.3 – Thick Field Oxide device - TFO

2.4 – Silicon Controlled Rectifier - SCR

# 1. Overview of ESD

 

## **ESD – Electrostatic Discharge**

- A sudden flow of electricity between 2 electrically charged objects caused by contact.
- Occur only when the *voltage differential between 2 objects is sufficiently high*.


---> **High voltage** and **large current** due to ESD can destroy gate oxide, metal line and junction.

## **ESD can occur in one of following ways:**

- a charged body touches an IC
- a charged IC touches a grounded surface.
- a charged machine touches an IC.
- an electrostatic field induces a voltage across a dielectric sufficient to break it down.

→ Some additional devices are used to protect internal circuit from ESD event.

 To understand how these devices can protect circuit under ESD event, this material introduce 4 kinds of ESD protection device and their operation.



# Outline

## 1. Overview of ESD

## 2. ESD protection devices

2.1 – Diode

2.2 – MOSFET

2.3 – Thick Field Oxide device - TFO

2.4 – Silicon Controlled Rectifier - SCR

## 3. Conclusion

## 2. ESD protection device


### *Purpose:*

- Providing a *low-impedance path* from input to supply *during ESD event* → absorb current.
- Providing a *very high impedance* (\*) during *normal operating condition* → don't affect circuit performance.
- Clamping input voltage at a safe level - below the dielectric breakdown voltage of gate-oxide.

(\*) - ESD device connect to: + the thin gate of input buffer trans → require high impedance input.  
+ the drain of output buffer trans → require low impedance output.
 
## 2. ESD protection device

**Characterizing ESD device:** extract I-V (current vs. voltage) curve of ESD device.



***I-V curve of NMOS trans under a positive ESD pulse***

$V_{\text{t1}}, I_{\text{t1}}$  - snapback trigger point

$V_{\text{SB}}$  - snapback voltage

$R_{\text{SB}}$  - on resistance

$V_{\text{t2}}, I_{\text{t2}}$  - 2<sup>nd</sup> breakdown trigger point

There 4 main models to do that:

- Human Body Model – HBM
- Machine Model – MM
- Charged Device Model – CDM
- **Transmission Line Pulsing – TLP ← widely accepted model**

(See more detail at Appendix)

# Outline

## 1. Overview of ESD

## 2. ESD protection devices

2.1 – Diode

2.2 – MOSFET

2.3 – Thick Field Oxide device - TFO


2.4 – Silicon Controlled Rectifier – SCR

## 3. Conclusion


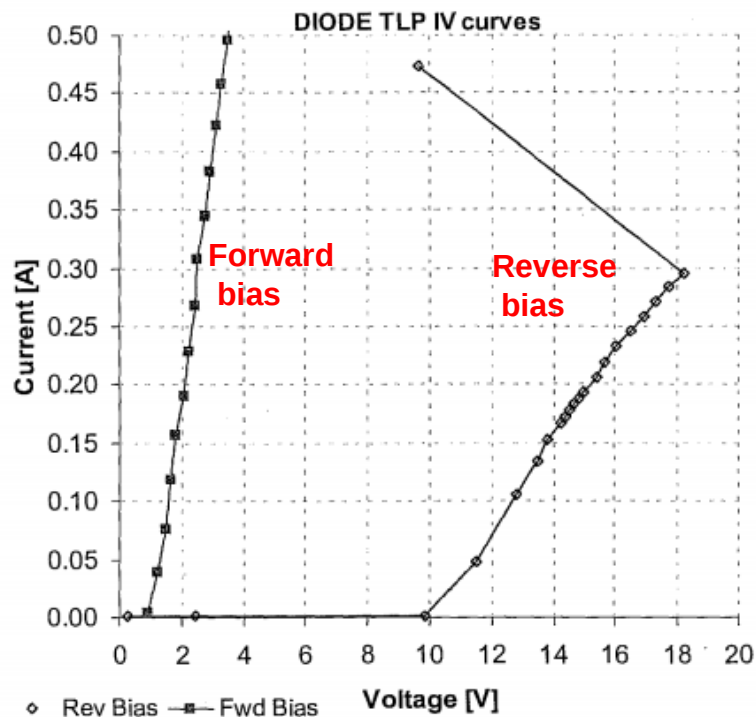
## 2.1 - ESD protection device – Diode (1/2)

- The most simple ESD protection device.
- Formed by N+ diffusion on P-sub **or** P+ diffusion on N-well.
- Must be in **reverse bias**.




I-V curve (TLP) of a diode

**Forward bias:**

Clamp voltage: ~ 1V

**Reverse bias:**


Snapback voltage: ~ 10V

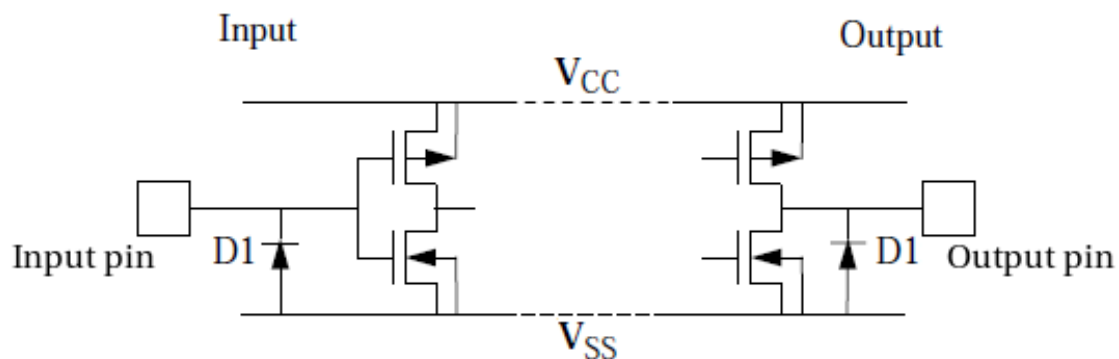

Example of using diode as ESD protection device


## 2.1 - ESD protection device - Diode (2/2)

### Positive pulse

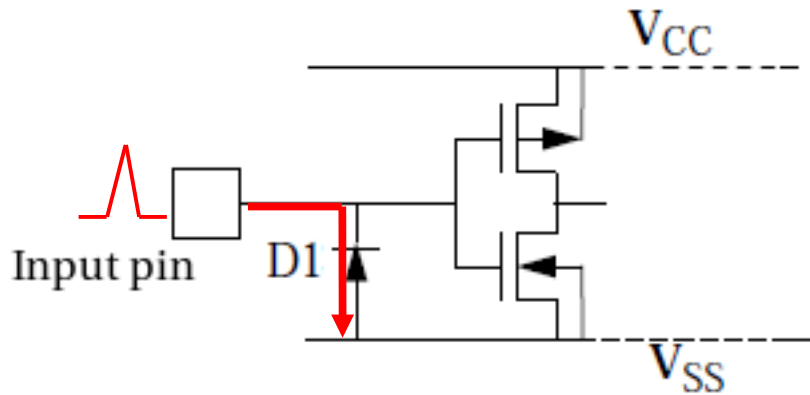

- Input voltage is clamped at breakdown voltage of D1

### Negative pulse

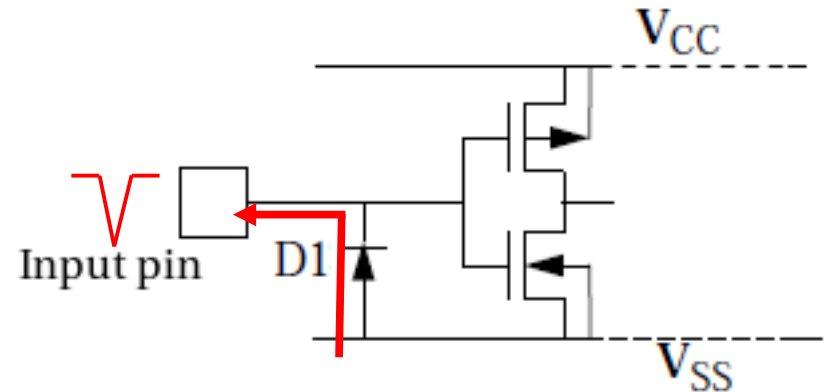

- Input voltage is clamped at -0.6V

### Advantage:

- Simple to implement.


### Disadvantage:

- High breakdown voltage
- Cannot breakdown quickly enough to protect a circuit from a fast-rising pulse.


## 2.2 - ESD protection device – MOSFET (1/3)
 
### NMOS:

- Drain is connected to input/output terminal.
- Gate & Source are connect to GND → NMOS is **OFF** at normal operation.
- When ESD occurs, conduction of parasitic npn bipolar trans will protect internal circuit.



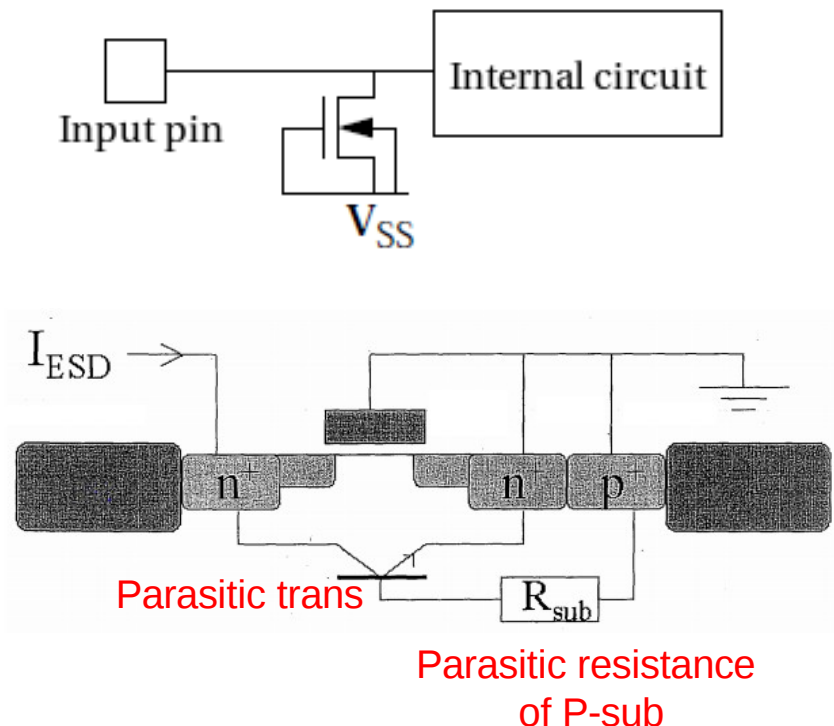
I-V curve of NMOS under positive ESD pulse



## 2.2 - ESD protection device – MOSFET (2/3)

- High positive pulse of ESD occurs → drain-substrate junction is broken down due to impact-ionization (\*)
- New free holes are attracted to GND through Source and P+ terminal → current flow occurs.
- When  $V_{BE} > 0.6V$ , npn transistor turns on
  - allow large current from collector to emitter of bipolar trans.
  - drain voltage of MOS is clamped at  $V_{CE}$  of bipolar trans.

==> Internal circuit is protected.

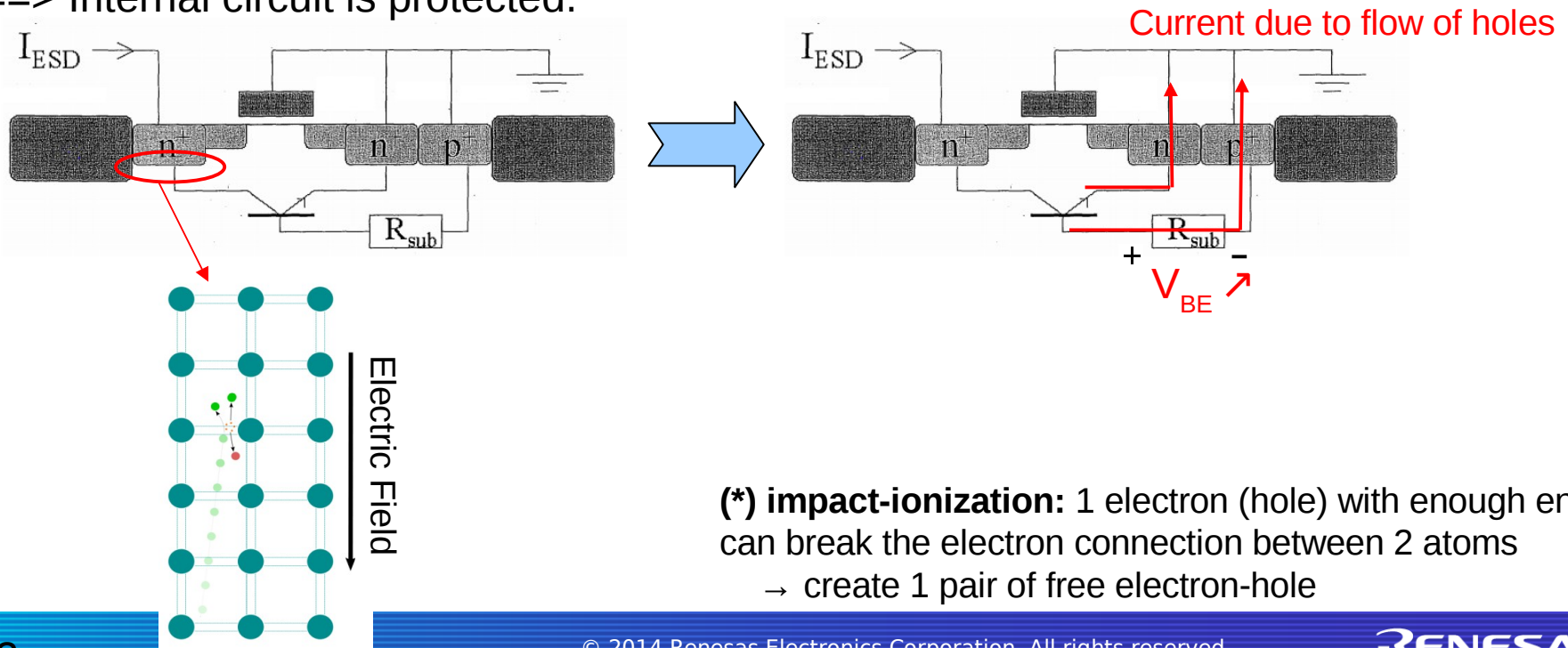

(\*) **impact-ionization:** 1 electron (hole) with enough energy can break the electron connection between 2 atoms  
→ create 1 pair of free electron-hole

## 2.2 - ESD protection device – MOSFET (3/3)

### *Advantage:*

- Can be turn-on more quickly (comparing with diode) at a lower voltage by using a gate-bouncing technique (*See detail at Appendix*).
- Using standard chip process without additional implant or masking steps.

### *Disadvantage:*

*Become unsuitable with recent technology*

- *Because of LDD structure, current drive capability of parasitic lateral BJT is reduced. This causes breakdown voltage higher*



**LDD:** Lightly Drop Drain

## 2.3 - ESD protection device – TFO

### Thick Field Oxide device – TFO:

- This is very old device structure to prevent ESD (about 1980s).
- Nowadays performance of this device was found to decrease significantly due to new process or techniques (STI, Lightly Doped Drain...).
- In modern process, particularly on high voltage pins, this device is still being used.

TLP curves of a W=80um, L=2um TFO.

 
 


Cross section of Thick Field Oxide device

Operation under ESD event is similar to NMOS device.

## 2.3 - ESD protection device – SCR (1/2)

### Silicon Controlled Rectifier – SCR:

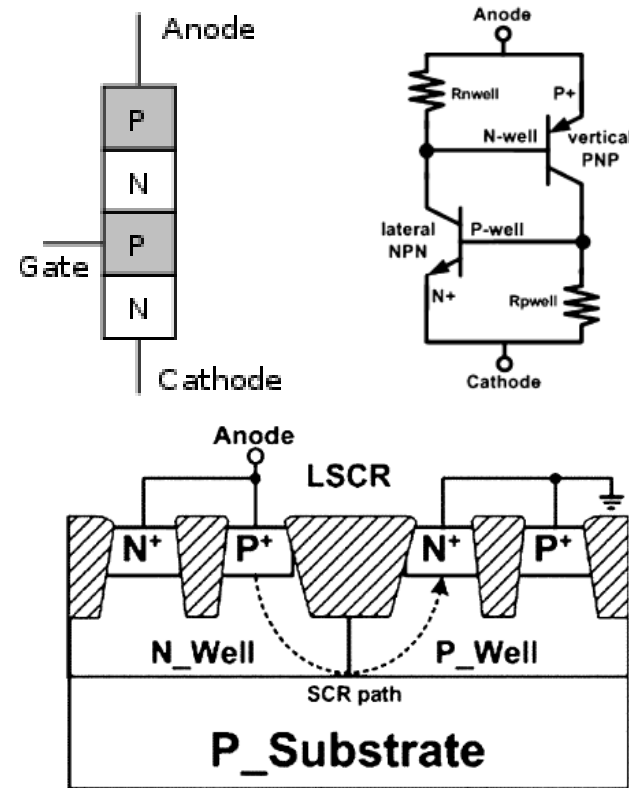 

**LSCR:** Lateral SCR



### Advantage:

- Low snapback voltage → low power dissipation.
- Can sustain higher level of ESD level within small layout area.

### Disadvantage:

- Easy to cause latch-up problem ← can be eliminated (See Appendix).
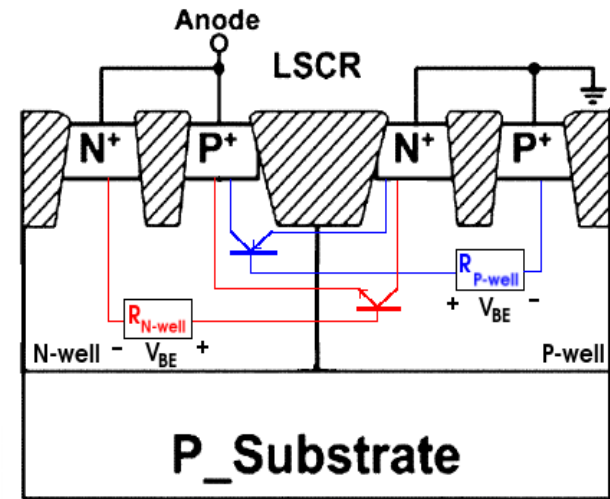 
## 2.3 - ESD protection device – SCR (2/2)



- High voltage applies to junction of Nwell – Pwell.
  - impact-ionization creates more free electron – hole pairs.
- Electrons are attracted to Anode  
Holes are attracted to Cathode

- When voltage drops through  $R_{P\text{-well}}$  ( or  $R_{N\text{-well}}$  ) larger than 0.6V  $\rightarrow$  parasitic pnp (or npn) bipolar transistor is ON.
- $\Rightarrow$  Conduct large current
- Clamp voltage between Anode – Cathode at  $V_{CE}$  of bipolar transistors.



### 3 - Conclusion

ESD device	Advantage	Disadvantage
Diode	- Simple to implement.	- High breakdown voltage. - Cannot breakdown quickly.
CMOS	- Can be turn-on quickly. - Simple to implement.	- Hot carrier relaxation (LDD) makes trade-off with ESD.
TFO	- Apply on high voltage pin.	- Performance decreases significantly with current process.
SCR	- Low snapback voltage (low power dissipation) - Sustain higher level of ESD.	- Latch-up problem.


- The protection method explained here are general ones.
  - Depending on process technology/device structure, practical measure differs.
- So we have to take care of the latest information.

# Thank you for your listening




# Appendix (1/3)

 
## Models used to obtain I-V curve of ESD device




Human Body Model - HBM

 

Machine Model – MM

 


Charged Device Model - CDM

 

Transmission Line Pulsing - TLP

## Appendix (2/3)

### Gate-bouncing technique

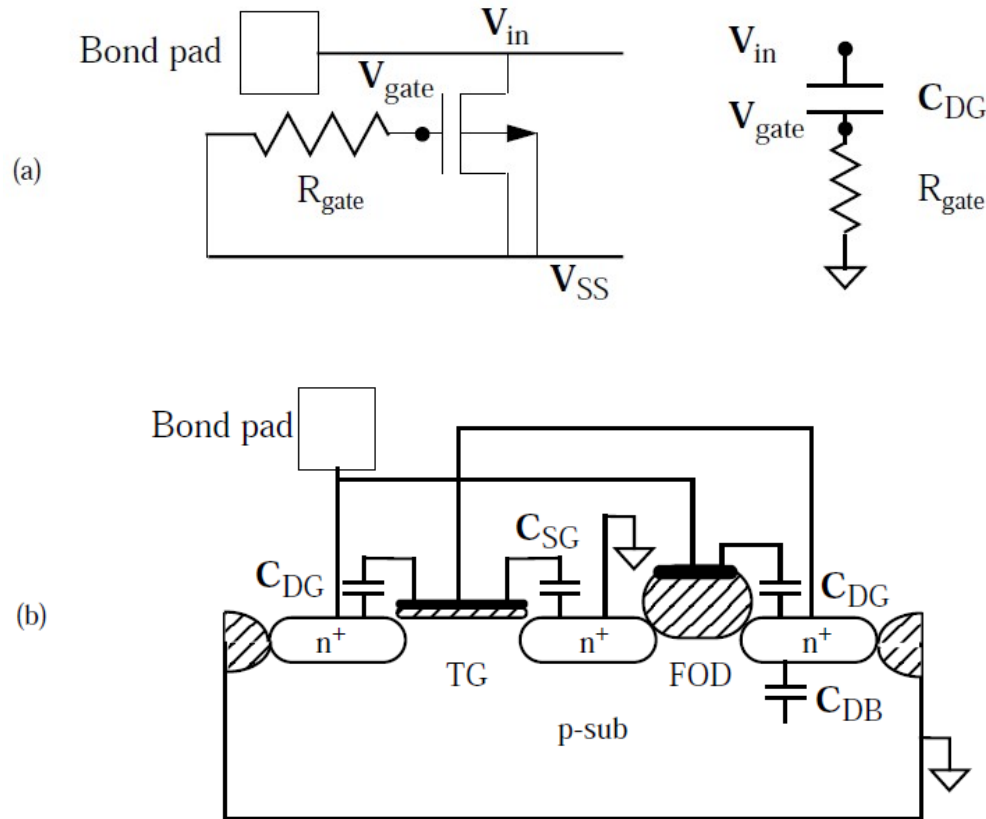

*Gate-bouncing techniques: (a) employment of a gate-bounce resistor and equivalent circuit; (b) dynamic gate coupling method.*


## Appendix (3/3)

### Methods to eliminate latch-up problem for SCR ESD device

There are 2 solutions to avoid the SCR with low switching voltage being accidentally triggered on by noise pulse when CMOS ICs are in normal circuit operating condition.

#### Method 1:

Increasing the triggering current of SCR

 

#### Method 2:

Increase holding voltage of SCR to be greater than VDD

